

به نام خدا


# زبان انتقال ثبات

RTL

Dr. Aref Karimiasfar  
A.karimiasfar@iut.ac.ir



# CPU

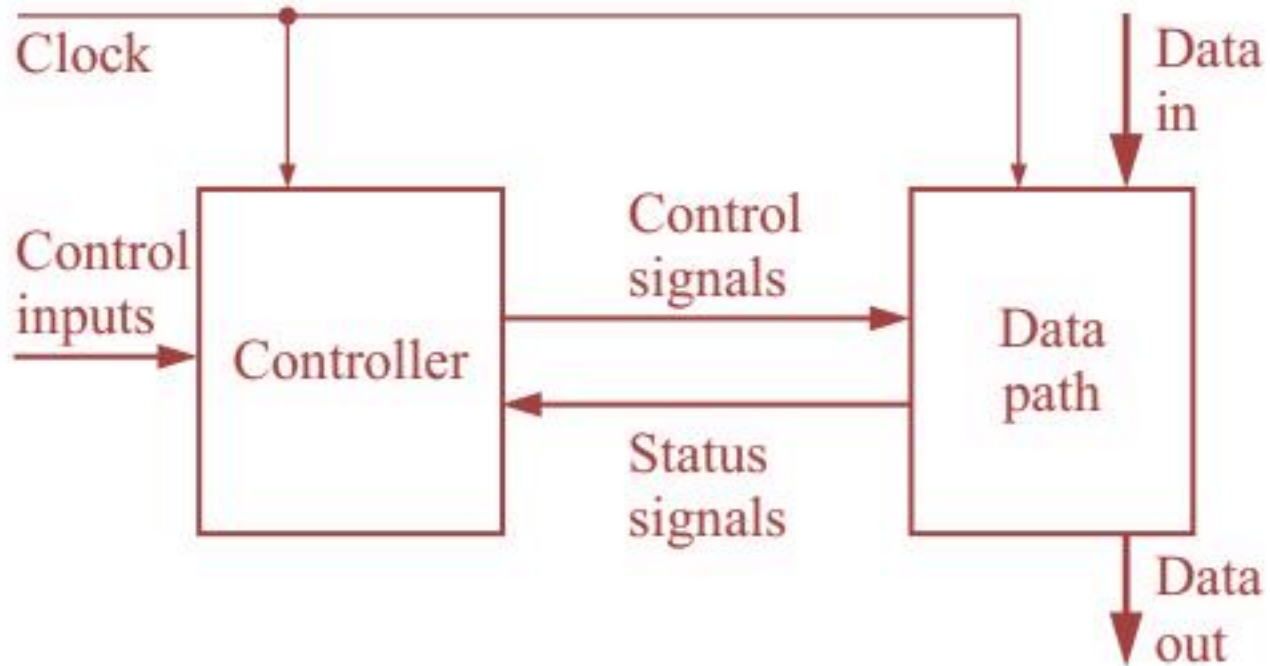


# Register Transfer Language (RTL)

- Digital System: An interconnection of hardware modules that do a certain task on the information.
- Registers + Operations performed on the data stored in them = Digital Module
- Modules are interconnected with common data and control paths to form a digital computer system
 
# Register Transfer Language cont.

- Microoperations: operations executed on data stored in one or more registers.
- For any function of the computer, a sequence of microoperations is used to describe it
- The result of the operation may be:
  - replace the previous binary information of a register
  - transferred to another register



# Register Transfer Language cont.

- The internal hardware organization of a digital computer is defined by specifying:
  - The set of registers it contains and their function
  - The sequence of microoperations performed on the binary information stored in the registers
  - The control that initiates the sequence of microoperations
- Registers + Microoperations Hardware + Control Functions = Digital Computer

# Register Transfer Language cont.

- Register Transfer Language (RTL) : a symbolic notation to describe the microoperation transfers among registers

Next steps:


- Define symbols for various types of microoperations,
- Describe the hardware that implements these microoperations

# Register Transfer (our first microoperation)


- Computer registers are designated by capital letters (sometimes followed by numerals) to denote the function of the register
  - R1: processor register
  - MAR: Memory Address Register (holds an address for a memory unit)
  - PC: Program Counter
  - IR: Instruction Register
  - SR: Status Register
 
# Register Transfer cont.

- The individual flip-flops in an n-bit register are numbered in sequence from 0 to n-1 (from the right position toward the left position)



Register R1

 


Showing individual bits

**A block diagram of a register**



 
# Register Transfer cont.

Other ways of drawing the block diagram of a register:




Numbering of bits

 

Partitioned into two parts
 
# Register Transfer cont.

- Information transfer from one register to another is described by a *replacement operator*:  $R2 \leftarrow R1$ 
  - This statement denotes a transfer of the content of register R1 into register R2
- The transfer happens in one clock cycle
- The content of the R1 (source) does not change
- The content of the R2 (destination) will be lost and replaced by the new data transferred from R1
- We are assuming that the circuits are available from the outputs of the source register to the inputs of the destination register, and that the destination register has a parallel load capability



# Register Transfer cont.

- Conditional transfer occurs only under a control condition

*If ( $P = 1$ ) then ( $R2 \leftarrow R1$ )*

- Representation of a (conditional) transfer


$P:$   $R2 \leftarrow R1$

- A binary condition ( $P$  equals to 0 or 1) determines when the transfer occurs
- The content of  $R1$  is transferred into  $R2$  only if  $P$  is 1


# Register Transfer cont.

Hardware implementation of a controlled transfer:  $P: R2 \leftarrow R1$

Block diagram:

 

Timing diagram

 


# Register Transfer cont.

Example:

P:  $R1 \leftarrow R2, R2 \leftarrow R1$

Block diagram:

 

Example:


P:  $R1 \leftarrow 0, R2 \leftarrow R1$

P:  $R1 \leftarrow 0, R1 \leftarrow R2$  ❌

# Register Transfer cont.

Basic Symbols for Register Transfers		
Symbol	Description	Examples
Letters & numerals	Denotes a register	MAR, R2
Parenthesis ( )	Denotes a part of a register	R2(0-7), R2(L)
Arrow $\leftarrow$	Denotes transfer of information	$R2 \leftarrow R1$
Comma ,	Separates two microoperations	$R2 \leftarrow R1, R1 \leftarrow R2$

# Bus and Memory Transfers

 



$$n(n-1)$$

# Bus and Memory Transfers cont.

- Paths must be provided to transfer information from one register to another
- A *Common Bus System* is a scheme for transferring information between registers in a multiple-register configuration
- A bus: set of common lines, one for each bit of a register, through which binary information is transferred one at a time
- Control signals determine which register is selected by the bus during each particular register transfer



# Bus and Memory Transfers cont.

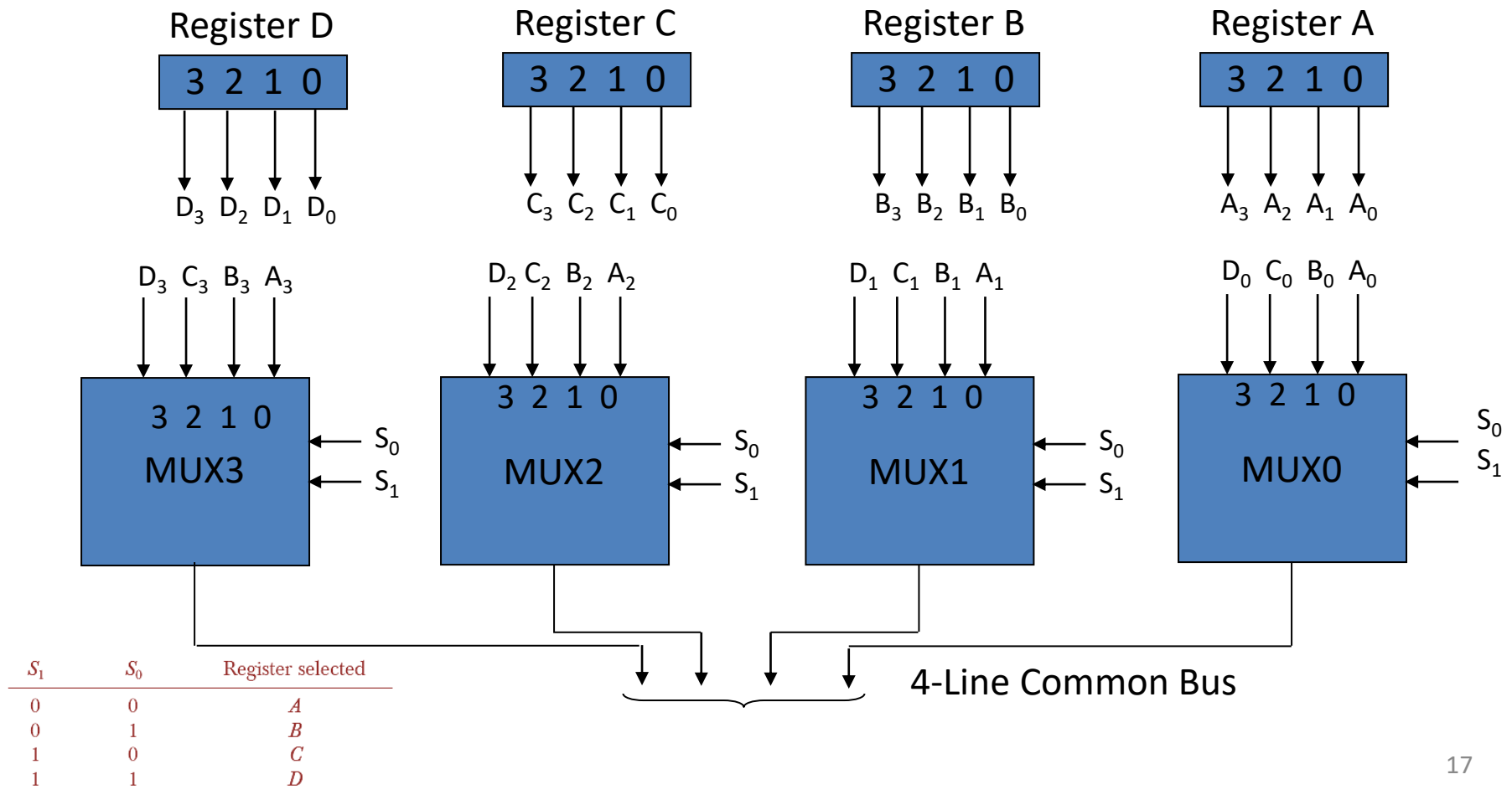 


# Bus and Memory Transfers cont.

- The transfer of information from a bus into one of many destination registers is done:
  - By connecting the bus lines to the inputs of all destination registers and then:
  - activating the load control of the particular destination register selected
- We write:  $R2 \leftarrow C$  to symbolize that the content of register  $C$  is *loaded into* the register  $R2$  using the common system bus
- It is equivalent to:  
$$\begin{aligned} & \text{BUS} \leftarrow C, (\text{select } C) \\ & R2 \leftarrow \text{BUS} (\text{Load } R2) \end{aligned}$$

 
# Bus and Memory Transfers: Three-State Bus Buffers

- A bus system can be constructed with three-state buffer gates instead of multiplexers
- A three-state buffer is a digital circuit that exhibits three states: logic-0, logic-1, and high-impedance (Hi-Z)




**Three-State Buffer**
 
# Bus and Memory Transfers: Three-State Bus Buffers cont.


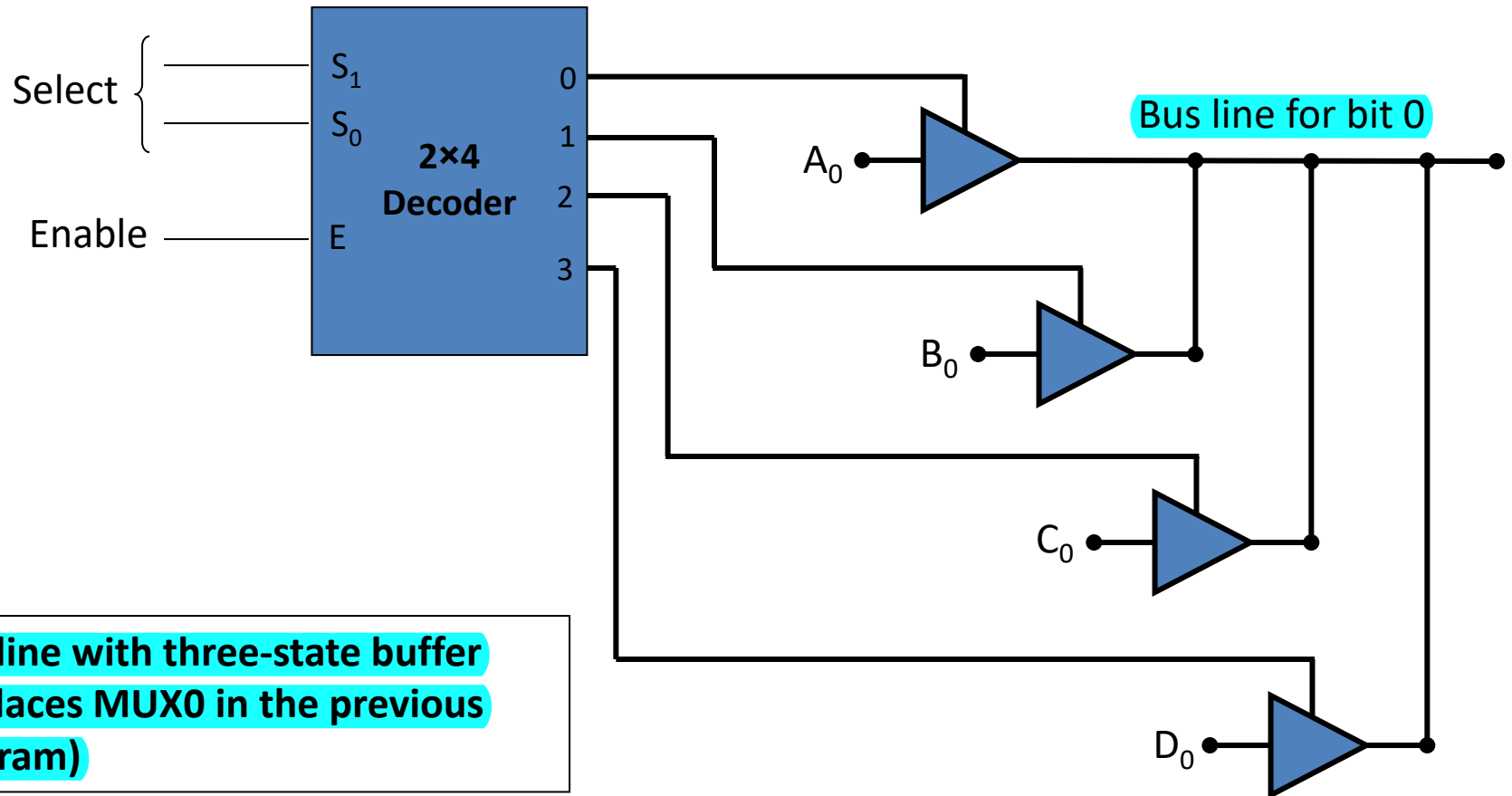
# Bus and Memory Transfers: Three-State Bus Buffers cont.




# Bus and Memory Transfers

- Memory read : Transfer from memory
- Memory write : Transfer to memory
- Data being read or wrote is called a memory word (called M)
- It is necessary to specify the address of M when writing /reading memory
- This is done by enclosing the address in square brackets following the letter M
- Example: M[0016] : the memory contents at address 0x0016

# Bus and Memory Transfers cnt.

- Assume that the address of a memory unit is stored in a register called the Address Register AR
- Lets represent a Data Register with DR, then:
  - Read:  $DR \leftarrow M[AR]$
  - Write:  $M[AR] \leftarrow DR$

# Bus and Memory Transfers cnt.

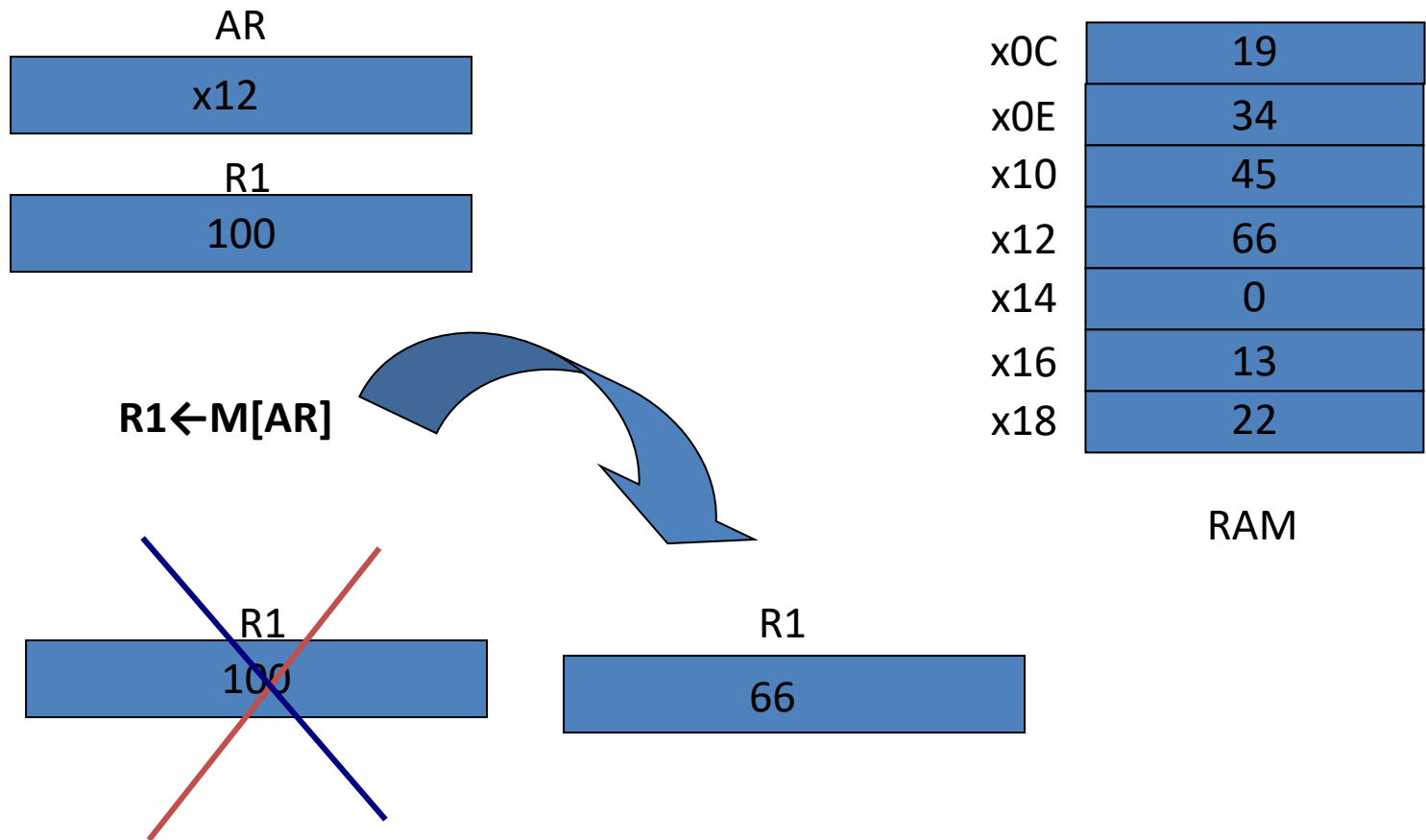



# Arithmetic Microoperations

- The microoperations most often encountered in digital computers are classified into four categories:
  - Register transfer microoperations
  - Arithmetic microoperations (on numeric data stored in the registers)
  - Logic microoperations (bit manipulations on non-numeric data)
  - Shift microoperations
- Register transfer microoperation
  - Does not change the information content
  - Other three types of microoperations change the information content

# Arithmetic Microoperations cont.

- The basic arithmetic microoperations are: addition, subtraction, increment, decrement, and shift
- Addition Microoperation:

$$R3 \leftarrow R1 + R2$$

- Subtraction Microoperation:

$$R3 \leftarrow R1 - R2 \text{ or :}$$

$$R3 \leftarrow R1 + \overline{R2} + 1$$

1's complement

# Arithmetic Microoperations cont.

- One's Complement Microoperation:

$$R2 \leftarrow \overline{R2}$$

- Two's Complement Microoperation:

$$R2 \leftarrow \overline{R2} + 1$$

- Increment Microoperation:

$$R2 \leftarrow R2 + 1$$

- Decrement Microoperation:

$$R2 \leftarrow R2 - 1$$

# Arithmetic Microoperations cont.

## Arithmetic Microoperations


Symbolic designation	Description
$R3 \leftarrow R1 + R2$	Contents of $R1$ plus $R2$ transferred to $R3$
$R3 \leftarrow R1 - R2$	Contents of $R1$ minus $R2$ transferred to $R3$
$R2 \leftarrow \overline{R2}$	Complement the contents of $R2$ (1's complement)
$R2 \leftarrow \overline{R2} + 1$	2's complement the contents of $R2$ (negate)
$R3 \leftarrow R1 + \overline{R2} + 1$	$R1$ plus the 2's complement of $R2$ (subtraction)
$R1 \leftarrow R1 + 1$	Increment the contents of $R1$ by one
$R1 \leftarrow R1 - 1$	Decrement the contents of $R1$ by one

# Hardware Implementation

## Arithmetic Microoperations

Arithmetic Circuit Function Table

Select			Input $Y$	Output $D = A + Y + C_{in}$	Microoperation
$S_1$	$S_0$	$C_{in}$			
0	0	0	$B$	$D = A + B$	Add
0	0	1	$B$	$D = A + B + 1$	Add with carry
0	1	0	$\bar{B}$	$D = A + \bar{B}$	Subtract with borrow
0	1	1	$\bar{B}$	$D = A + \bar{B} + 1$	Subtract
1	0	0	0	$D = A$	Transfer $A$
1	0	1	0	$D = A + 1$	Increment $A$
1	1	0	1	$D = A - 1$	Decrement $A$
1	1	1	1	$D = A$	Transfer $A$

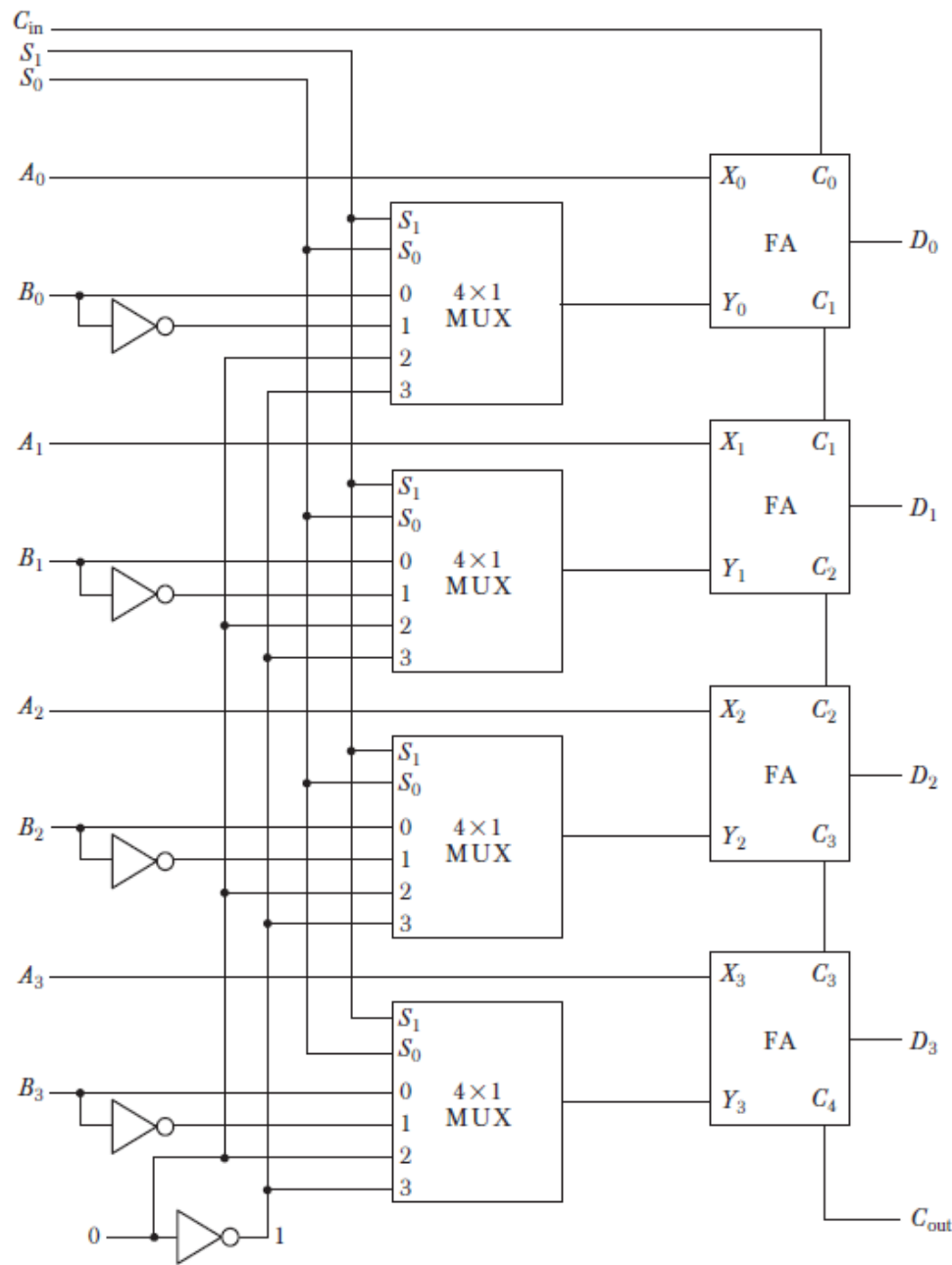

# Logic Microoperations

- Logic microoperations specify binary operations for strings of bits stored in registers
  - These operations consider each bit of the register separately and treat them as binary variables
- Example:
  - Exclusive-or microoperation with the contents of two registers R1 and R2 is symbolized by

$$P: R1 \leftarrow R1 \oplus R2$$


# Logic Microoperations

Sixteen Logic Microoperations

Boolean function	Microoperation	Name
$F_0 = 0$	$F \leftarrow 0$	Clear
$F_1 = xy$	$F \leftarrow A \wedge B$	AND
$F_2 = xy'$	$F \leftarrow A \wedge \bar{B}$	
$F_3 = x$	$F \leftarrow A$	Transfer $A$
$F_4 = x'y$	$F \leftarrow \bar{A} \wedge B$	
$F_5 = y$	$F \leftarrow B$	Transfer $B$
$F_6 = x \oplus y$	$F \leftarrow A \oplus B$	Exclusive-OR
$F_7 = x + y$	$F \leftarrow A \vee B$	OR
$F_8 = (x + y)'$	$F \leftarrow \overline{A \vee B}$	NOR
$F_9 = (x \oplus y)'$	$F \leftarrow \overline{A \oplus B}$	Exclusive-NOR
$F_{10} = y'$	$F \leftarrow \bar{B}$	Complement $B$
$F_{11} = x + y'$	$F \leftarrow A \vee \bar{B}$	
$F_{12} = x'$	$F \leftarrow \bar{A}$	Complement $A$
$F_{13} = x' + y$	$F \leftarrow \bar{A} \vee B$	
$F_{14} = (xy)'$	$F \leftarrow \overline{A \wedge B}$	NAND
$F_{15} = 1$	$F \leftarrow \text{all 1's}$	Set to all 1's

# Hardware Implementation Logic Microoperations

One stage of logic circuit.

 

(a) Logic diagram

$S_1$	$S_0$	Output	Operation
0	0	$E = A \wedge B$	AND
0	1	$E = A \vee B$	OR
1	0	$E = A \oplus B$	XOR
1	1	$E = \bar{A}$	Complement

(b) Functional table



# Shift Microoperations

- Shift microoperations are used for serial transfer of data
  - Also used in conjunction with arithmetic, logic, and other data-processing operations
- Contents of a register can be shifted to the left or the right
  - At the same time, the first flip-flop receives its binary information from the serial input

$R1 \leftarrow \text{shl } R1$

$R2 \leftarrow \text{shr } R2$

# Shift Microoperations cnt.


## Shift Microoperations

Symbolic designation	Description
$R \leftarrow \text{shl } R$	Shift-left register $R$
$R \leftarrow \text{shr } R$	Shift-right register $R$
$R \leftarrow \text{cil } R$	Circular shift-left register $R$
$R \leftarrow \text{cir } R$	Circular shift-right register $R$
$R \leftarrow \text{ashl } R$	Arithmetic shift-left $R$
$R \leftarrow \text{ashr } R$	Arithmetic shift-right $R$

# Hardware Implementation

## Shift Microoperations

Functional table				
Select	Output			
$S$	$H_0$	$H_1$	$H_2$	$H_2$
0	$I_R$	$A_0$	$A_1$	$A_2$
1	$A_1$	$A_2$	$A_3$	$I_L$

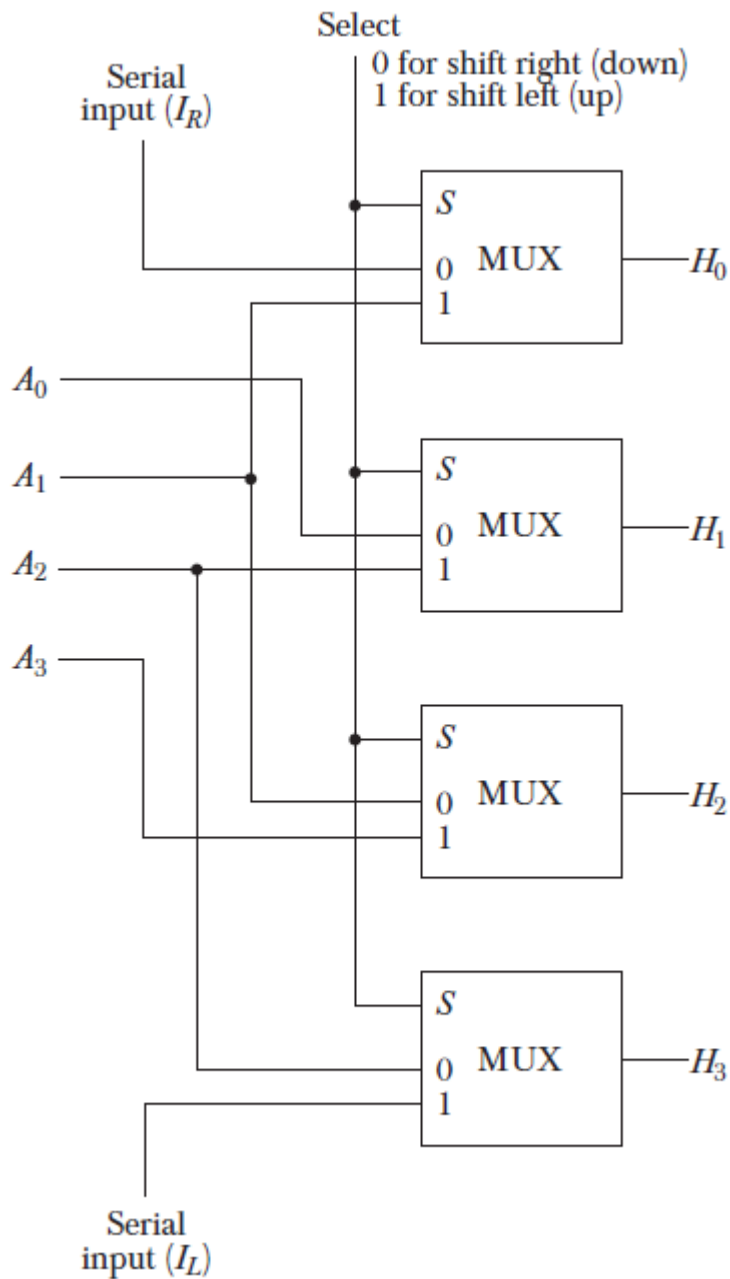

پایان

موفق و پیروز باشید