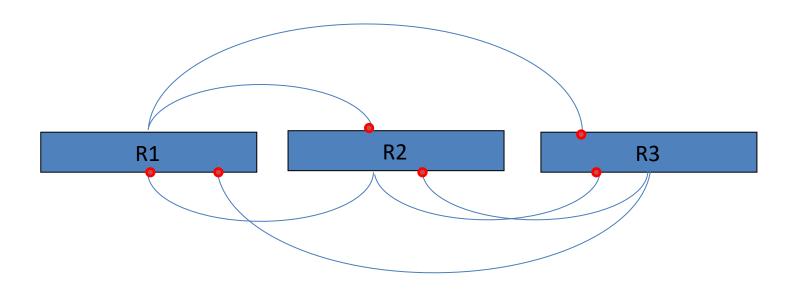
# سازمان داخلی کامپیوتر پایه


Dr. Aref Karimiafshar A.karimiafshar@iut.ac.ir




# مثال



$$R2 \leftarrow R1, R3 \leftarrow R2$$

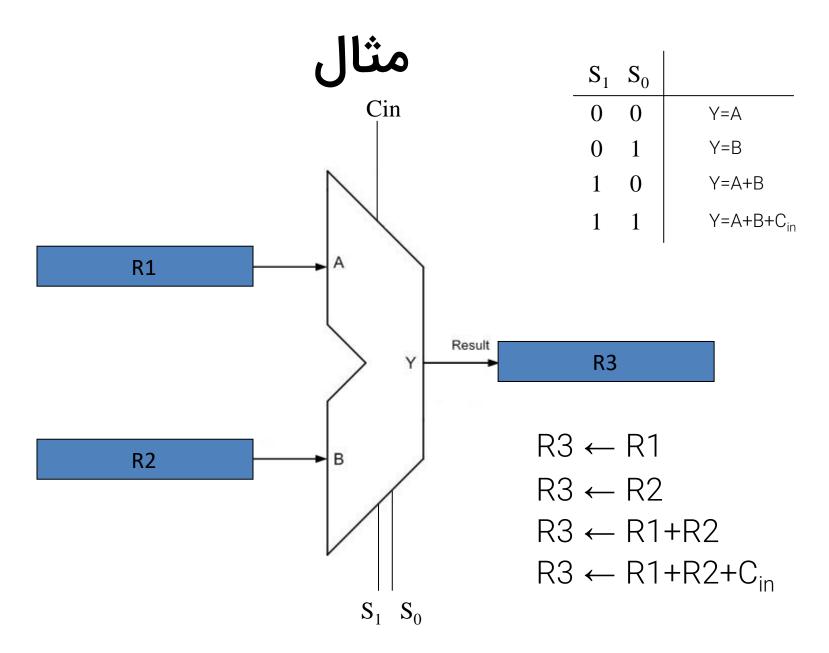

## مثال

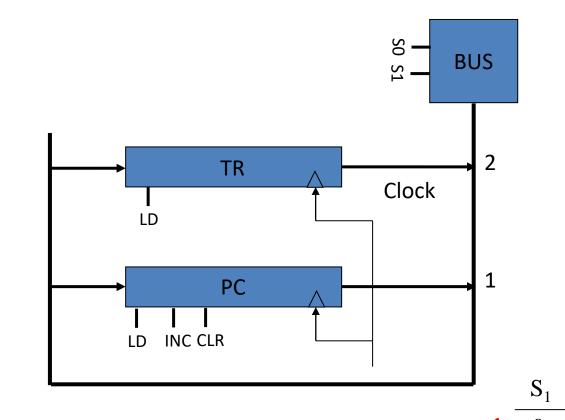

PC← 0

PC← TR

TR← PC

PC← PC+1

TR← PC+1 ×


PC← 1 '


BUS ← TR


**2**: 1

BUS ← PC


### **Timing and Control**

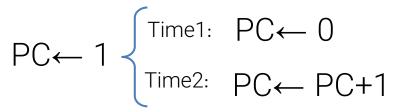

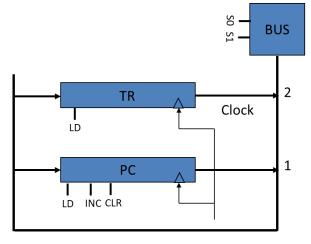


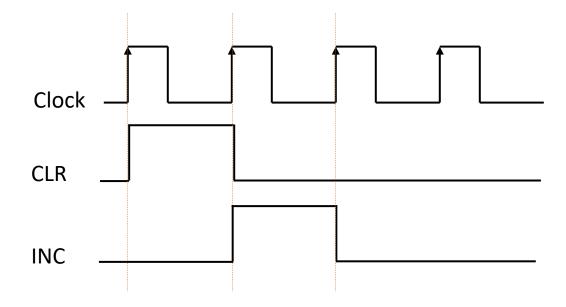


Timing and Control cnt.

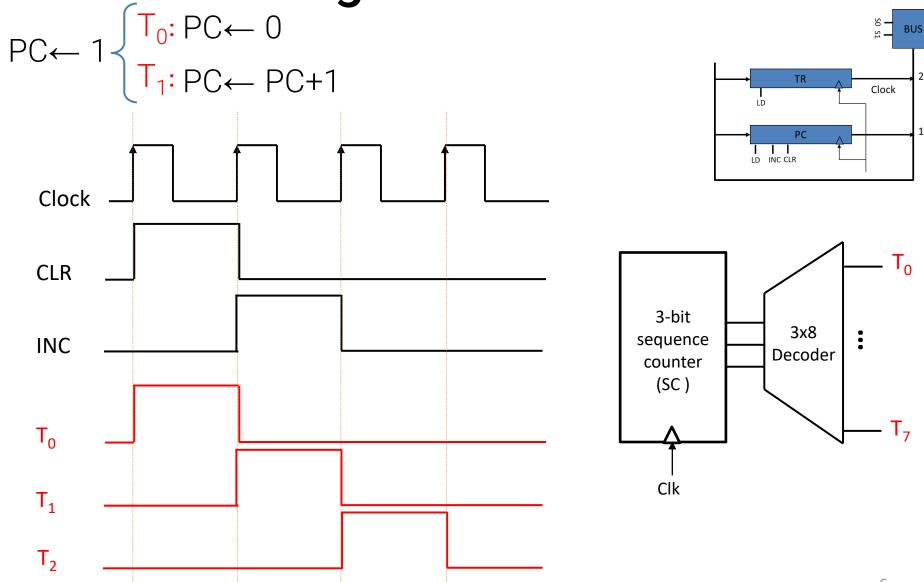


## **CPU**

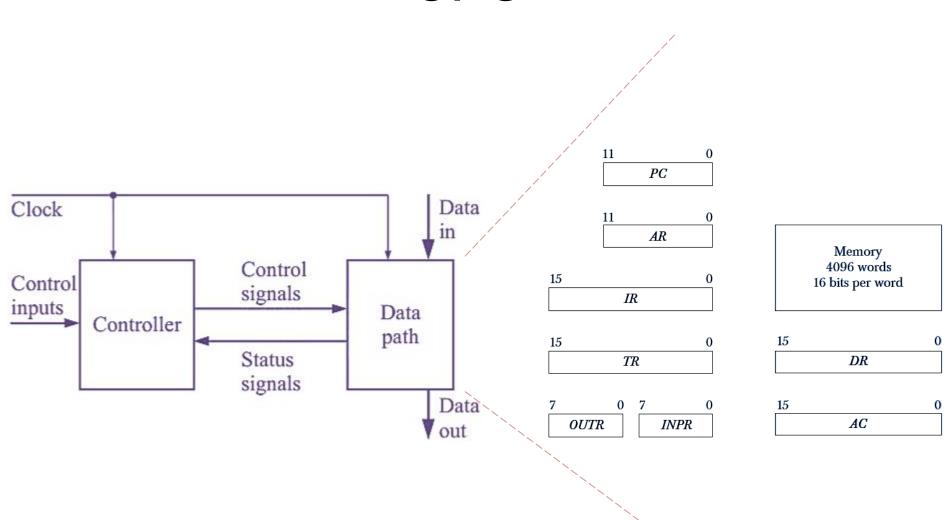


#### **Data Path**

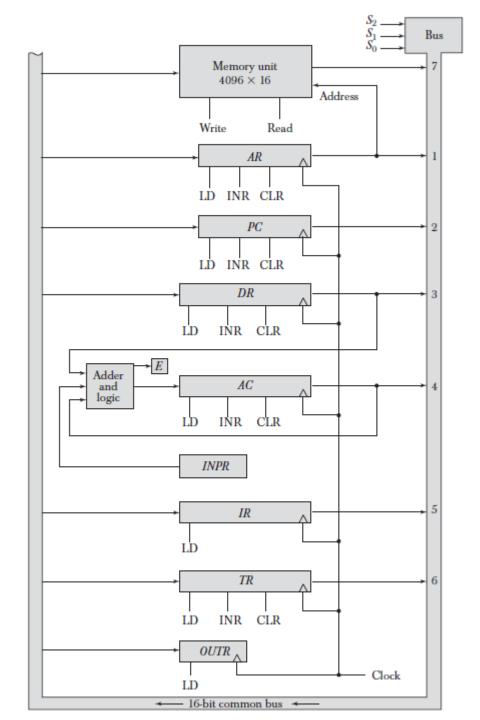

## Control unit of basic computer

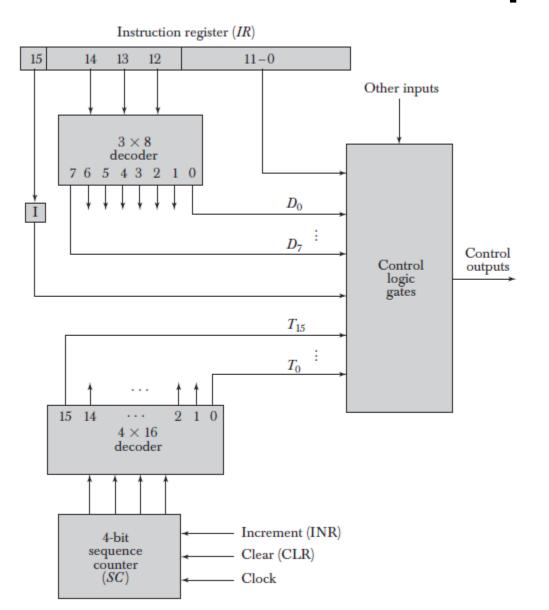

## Example of control timing signals

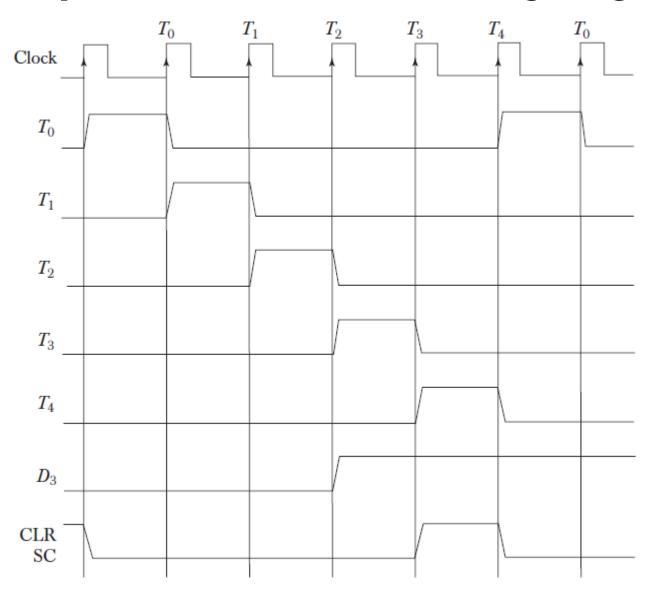

#### Control unit of basic computer

- Two major types of control organization
  - Hardwired control
  - Microprogrammed control
- Hardwired Organization
  - The control logic is implemented with gates, flip-flops, decoders, and other digital circuits
  - The advantage that it can be optimized to produce a fast mode of operation
- Microprogrammed Organization
  - The control information is stored in a control memory
  - Any required changes or modifications can be done by updating the microprogram in control memory

## پایان

موفق و پیروز باشید